

EXPERIMENT-02

AIM:

To simulate and synthesis ENCODER, DECODER, MULTIPLEXER, DEMULTIPLEXER, MAGNITUDE COMPARATOR using Xilinx ISE.

APPARATUS REQUIRED: Xilinx 14.7 Spartan6 FPGA

PROCEDURE:

STEP:1 Start the Xilinx navigator, Select and Name the New project.

STEP:2 Select the device family, device, package and speed.

STEP:3 Select new source in the New Project and select Verilog Module as the Source type.

STEP:4 Type the File Name and Click Next and then finish button. Type the code and save it.

STEP:5 Select the Behavioral Simulation in the Source Window and click the check syntax.

STEP:6 Click the simulation to simulate the program and give the inputs and verify the outputs as per the truth table.

STEP:7 Select the Implementation in the Sources Window and select the required file in the Processes Window.

STEP:8 Select Check Syntax from the Synthesize XST Process. Double Click in the FloorplanArea/IO/Logic-Post Synthesis process in the User Constraints process group. UCF(User constraint File) is obtained.


STEP:9 In the Design Object List Window, enter the pin location for each pin in the Loc column Select save from the File menu.

STEP:10 Double click on the Implement Design and double click on the Generate Programming File to create a bitstream of the design.(.v) file is converted into .bit file here.

STEP:11 On the board, by giving required input, the LEDs starts to glow light, indicating the output.

LOGIC DIAGRAM


ENCODER:

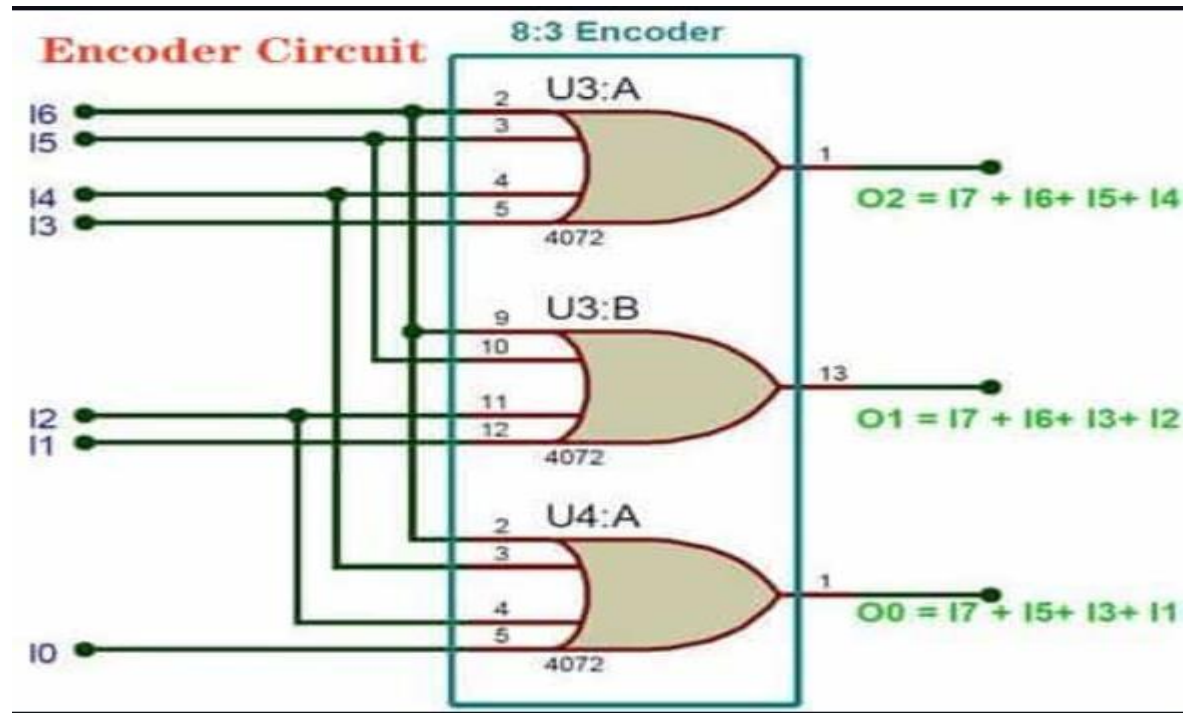


VERILOG CODE:

```
module encoder(i,o);
input [7:0]i;
output [2:0]o;
or g1(o[0],i[1],i[3],i[5],i[7]);
or g2(o[1],i[2],i[3],i[6],i[7]);
or g3(o[2],i[4],i[5],i[6],i[7]);
endmodule
```

OUTPUT:

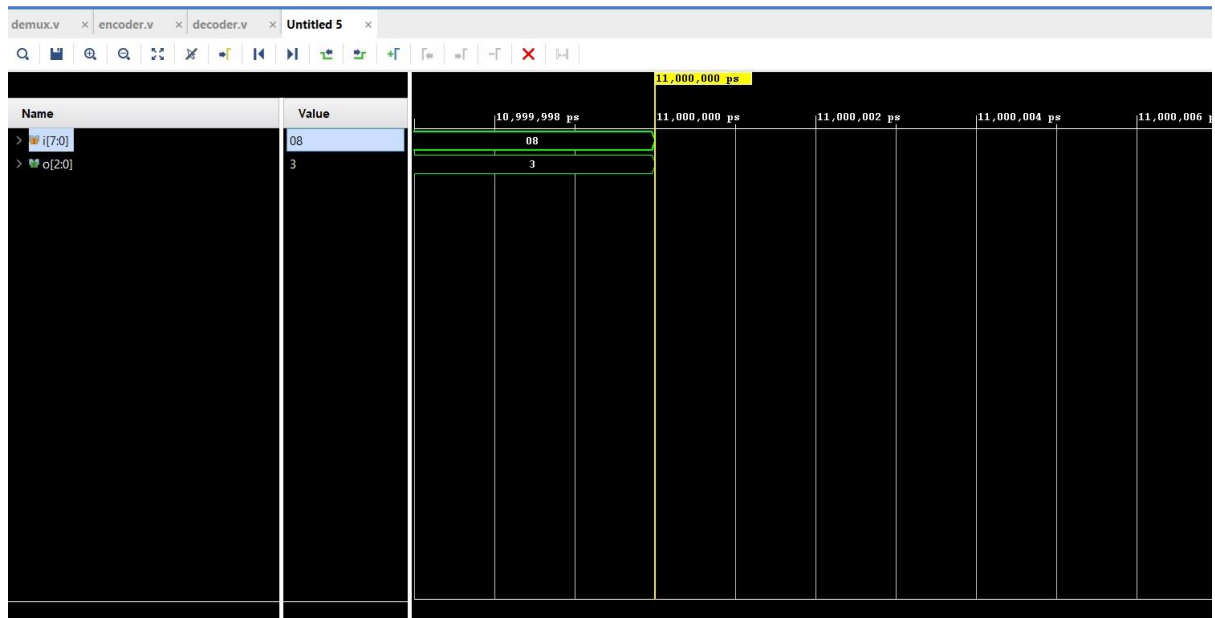


DECODER:

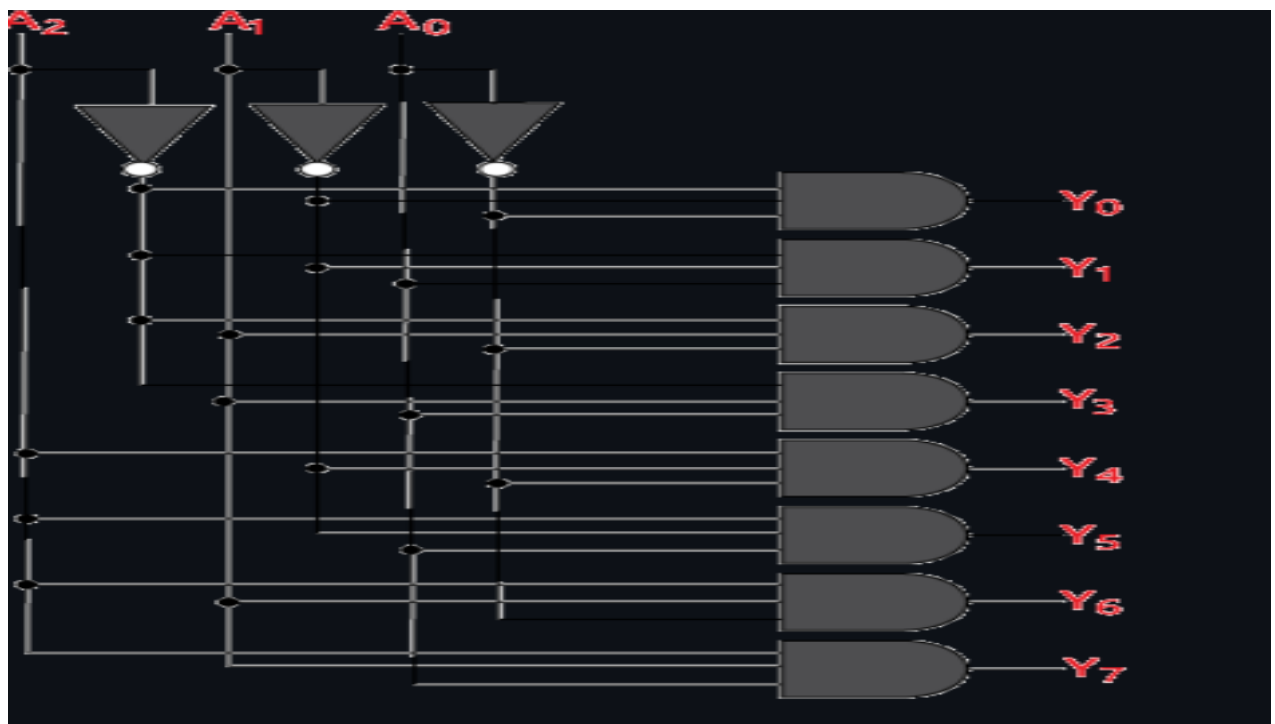


VERILOG CODE:

```
module decoder(a,y);  
MULTIPLEXERinput [2:0]a;  
output [7:0]y;  
wire w0,w1,w2;  
not g1(w0,a[0]);  
not g2(w1,a[1]);  
not g3(w2,a[2]);  
and g4(y[0],w0,w1,w2);  
and g5(y[1],w2,w1,a[0]);  
and g6(y[2],w2,a[1],w0);  
and g7(y[3],w2,a[1],a[0]);  
and g8(y[4],a[2],w1,w0);  
and g9(y[5],a[2],w1,a[0]);  
and g10(y[6],a[2],a[1],w0);  
and g11(y[7],a[2],a[1],a[0]);  
endmodule
```

OUTPUT:

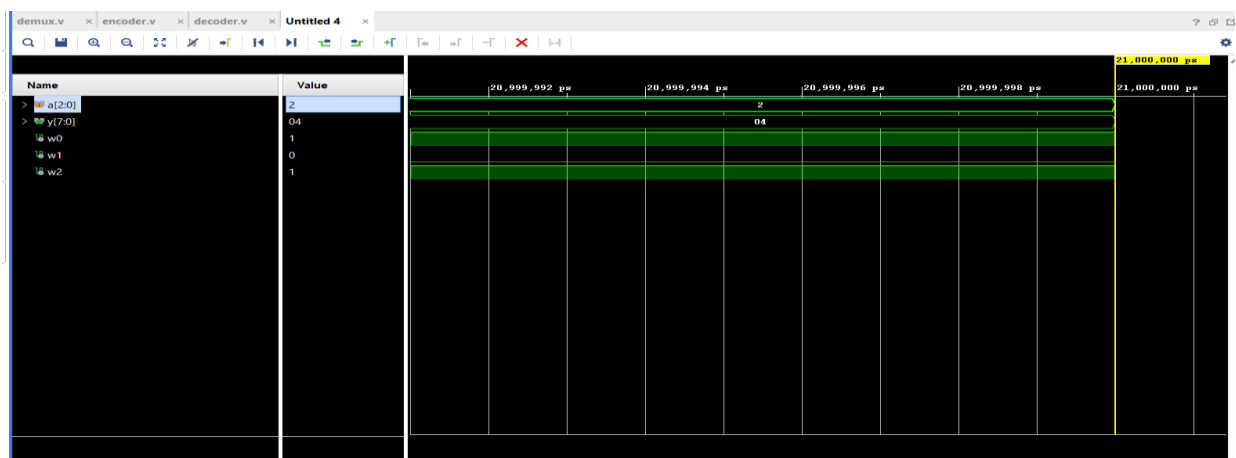

MULTIPLEXER:

 

VERILOG CODE:


```
module mux(d,s,y);
input[7:0]d;
input[2:0]s;
output y;
wire w1,w2,w3,w4,w5,w6,w7,w8,w9,w10,w11;
not g1 (w1,s[2]);
not g2(w2,s[1]);
not g3(w3,s[0]);
and g4(w4,w1,w2,w3,d[0]);
and g5(w5,w1,w2,s[0],d[1]);
and g6(w6,w1,w3,s[1],d[2]);
and g7(w7,w1,s[1],s[0],d[3]);
and g8(w8,w2,w3,s[2],d[4]);
and g9(w9,w2,s[2],s[0],d[5]);
and g10(w10,w3,s[1],s[2],d[6]);
```

```


and g11(w11,s[0],s[1],s[2],d[7]);
or g12(y,w4,w5,w6,w7,w8,w9,w10,w11);
endmodule

```

OUTPUT:

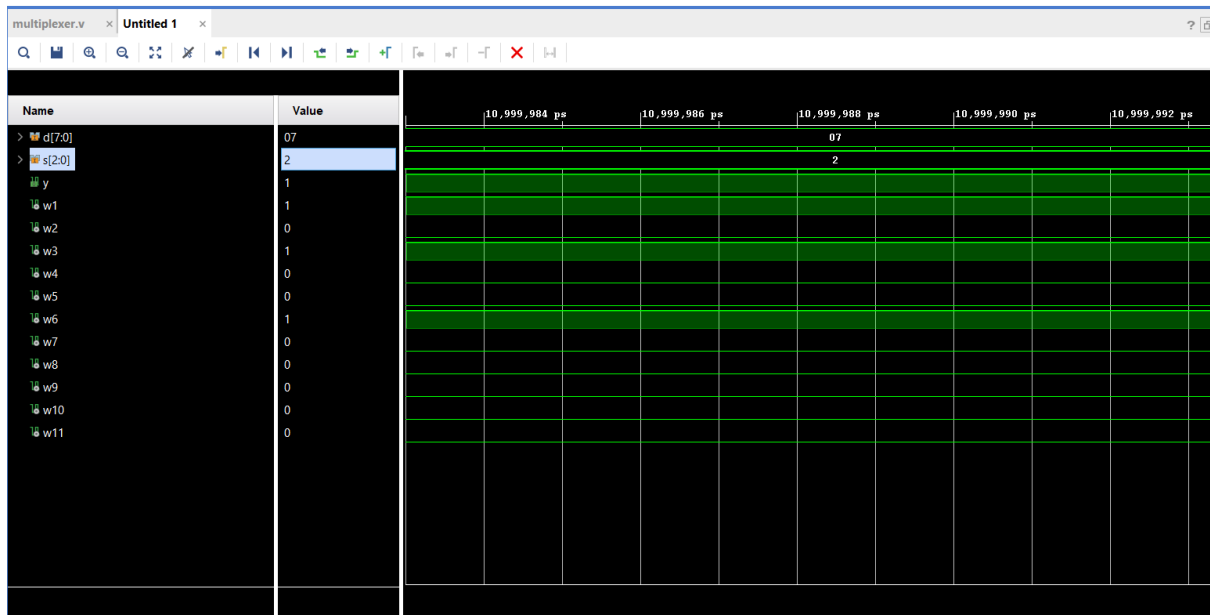


DEMULTIPLEXER:

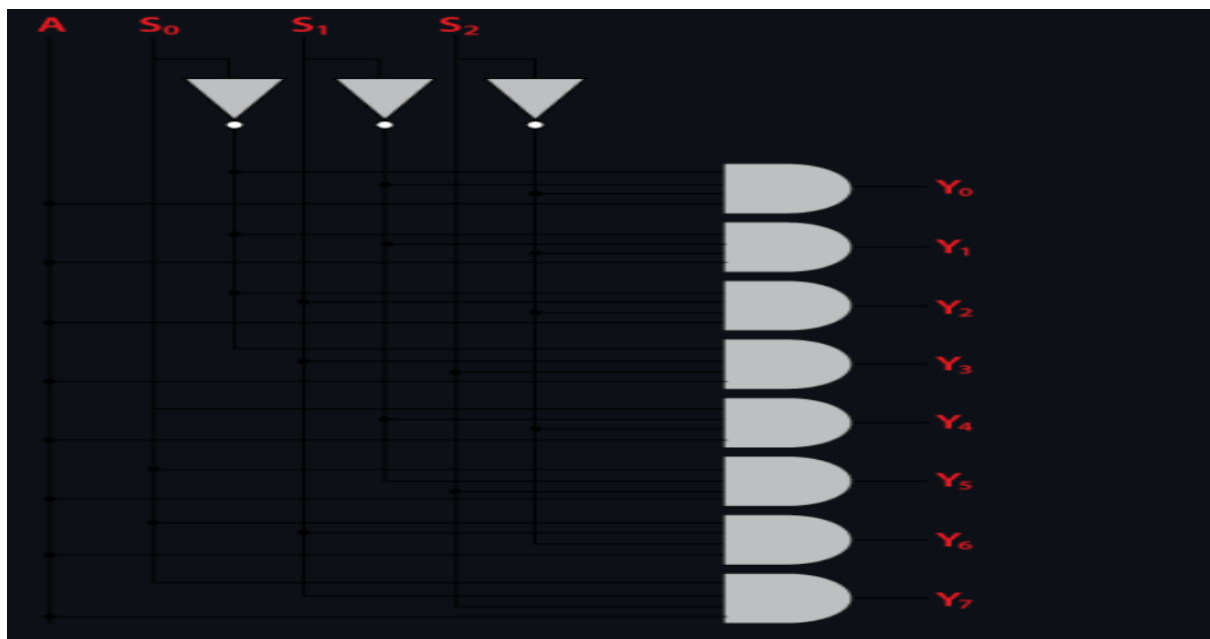

VERILOG CODE:

```
module demux8x1(d,s,y);
input d;
input [2:0]s;
output [7:0]y;
wire w1,w2,w3;
not g1(w1,s[0]);
not g2(w2,s[1]);
not g3(w3,s[2]);
and g4(y[0],d,w1,w2,w3);
and g5(y[1],d,w1,s[0],w3);
and g6(y[2],d,w3,s[1],w1);
and g7(y[3],d,s[0],s[1],w3);
and g8(y[4],d,s[2],w1,w2);
and g9(y[5],d,s[2],s[0],w2);
and g10(y[6],d,w1,s[1],s[2]);
and g11(y[7],d,s[2],s[1],s[0]);
endmodule
```

OUTPUT:

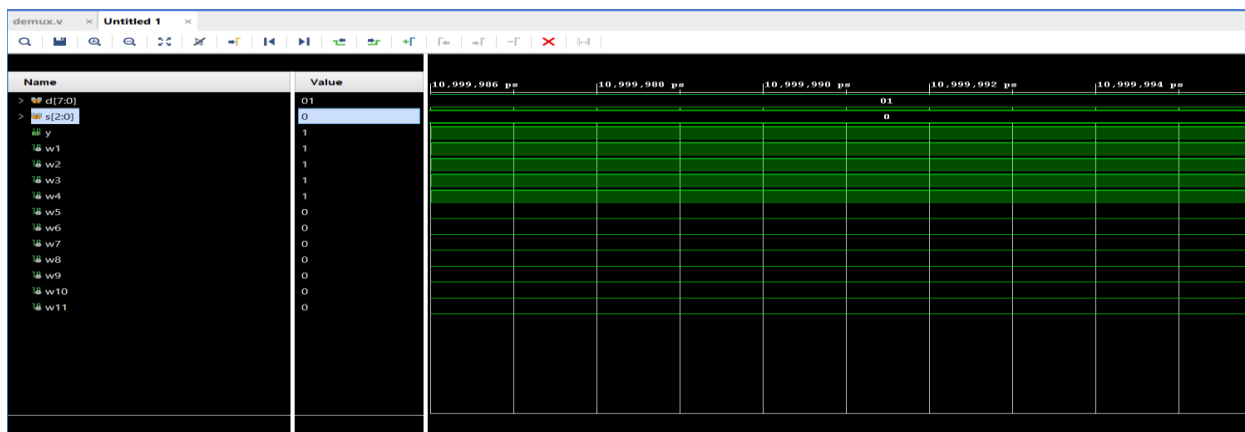

MAGNITUDE COMPARATOR:



VERILOG CODE:

```
module magnitude(a,b,greater,lesser,equal);
input[2:0]a,b;
output reg greater,lesser,equal;
always @(*)
begin
if (a>b)
begin
greater=1'b1;
lesser=1'b0;
equal=1'b0;
end
else if(a<b)
begin
greater=1'b0;
lesser=1'b1;
equal=1'b0;
end
else
```




```

begin
greater=1'b0;
lesser=1'b0;
equal=1'b1;
end
end
endmodule

```

OUTPUT:

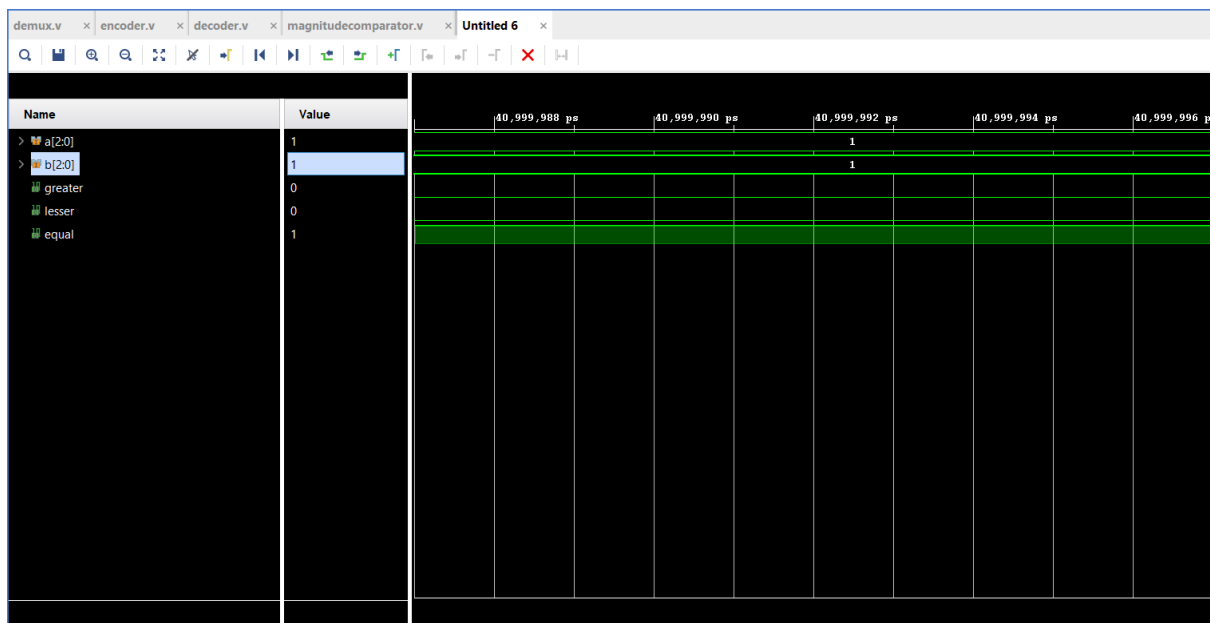

RESULT:

Thus ,the given encoder, decoder, multiplexer, demultiplexer, magnitude comparator are simulated and synthesis are executed successfully

